



北京理工大学
Beijing Institute of Technology

本科实验报告

实验名称：十六位加法器设计

课程名称：	集成电路设计实践（I）	实验时间：	2018/4/22
任课教师：	张蕾	实验地点：	综 A
实验教师：	张蕾	实验类型：	<input checked="" type="checkbox"/> 原理验证 <input type="checkbox"/> 综合设计 <input type="checkbox"/> 自主创新
学生姓名：	施念		
学号/班级：	1120161302/05011609	组 号：	
学 院：	信息与电子学院	同组搭档：	
专 业：	电子信息工程	成 绩：	

实验二 十六位加法器设计

一、实验目的

- (1) 掌握元件例化的方法
- (2) 理解 for/generate 语句的用法
- (3) 编程完成 4 位加法器和 16 位加法器的设计

二、实验原理

将 n 个加法器相连可得 n 位加法器，但是加法时间较长，解决的方法之一就是采用“超前进位加法器电路”来同时形成各位进位，从而实现快速加法。超前进位产生电路是根据各位进位的形成条件来实现的。

以一个四位超前进位加法器为例，首先需要做出两个传递函数：进位产生函数 P_i 和进位传送函数 Q_i 。

$$P_i = A_i \oplus B_i$$

$$Q_i = A_i \& B_i$$

如下图所示，为 4 位超前进位加法器内部逻辑图以及各个门所代表的含义，由下图可以写出各个进位输入的逻辑表达式

 


图 1 四位超前进位加法器内部逻辑图

 


图 2 逻辑门示意图

由上图可以写出各个进位输入的逻辑表达式：

$c(0) \leq \text{cin};$

$c(1) \leq (\text{cin and } p(0)) \text{ or } g(0);$

$c(2) \leq (\text{cin and } p(0) \text{ and } p(1)) \text{ or } (g(0) \text{ and } p(1)) \text{ or } g(1);$

$c(3) \leq (\text{cin and } p(0) \text{ and } p(1) \text{ and } p(2)) \text{ or } (g(0) \text{ and } p(1) \text{ and } p(2)) \text{ or } (g(1) \text{ and } p(2)) \text{ or } g(2);$

$c(4) \leq (\text{cin and } p(0) \text{ and } p(1) \text{ and } p(2) \text{ and } p(3)) \text{ or } (g(0) \text{ and } p(1) \text{ and } p(2) \text{ and } p(3)) \text{ or } (g(1) \text{ and } p(2) \text{ and } p(3)) \text{ or } (g(2) \text{ and } p(3)) \text{ or } g(3);$

而每位的输入可以写成表达式：

$$S_i = P_i \oplus C_i$$

二、实验内容

本次任务需要使用 VHDL 语言编写一个 16 位超前进位加法器，顶层模块的名字为 adder.vhd，建议调用四个子模块，每个子模块进行 4 位超前进位加法，最终整个设计完成 16 位加法。进行仿真时需要至少 4 个测试值，包含 cin 为高和低的情况。

16 位加法器的设计：

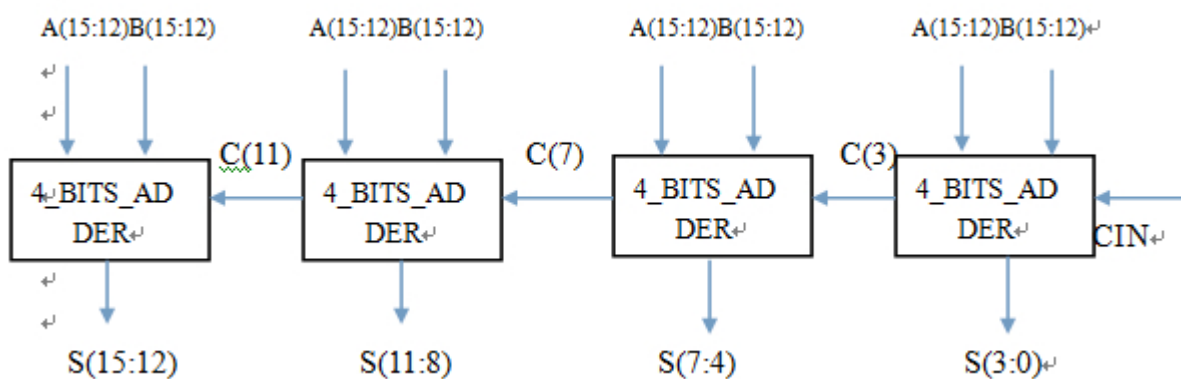


图 3 16 位加法器结构示意图

三、实验代码

```
-----adder_4.vhd-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity adder_4 is  
port (  
    a,b:in std_logic_vector(3 downto 0);  
    cin:in std_logic;  
    s:out std_logic_vector(3 downto 0);  
    cout: out std_logic  
);  
end entity adder_4;  
-----  
architecture behave of adder_4 is  
    signal c: std_logic_vector(4 downto 0);  
    signal p: std_logic_vector(3 downto 0) ;  
    signal g: std_logic_vector(3 downto 0) ;  
begin  
    -----  
    G1 : for i in 3 downto 0 generate  
        p(i) <= a(i) xor b(i);  
        g(i) <= a(i) and b(i);  
        s(i) <= p(i) xor c(i);  
    end generate G1;  
    -----  
    c(0) <= cin; --initialize c(0)  
    G2 : for j in 1 to 4 generate  
        c(j) <= (c(j-1) and p(j-1)) or g(j-1);  
    end generate G2;  
    cout <= c(4); -- cout  
end architecture behave;
```

```
-----adder.vhd-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity adder is  
    port (  
        a,b:in std_logic_vector(15 downto 0) ;
```

```

        s:out std_logic_vector(15 downto 0) ;
        cin: in std_logic;
        cout:out std_logic
    );
end entity adder;
-----

architecture behave of adder is
component adder_4 is
    port (
        a,b:in std_logic_vector(3 downto 0);
        s:out std_logic_vector(3 downto 0);
        cin:in std_logic;
        cout: out std_logic
    );
end component adder_4;
-----

signal m1, m2, m3:std_logic;
begin
u1:adder_4 port map(a(3 downto 0),b(3 downto 0),s(3 downto 0),cin,m1);
u2:adder_4 port map(a(7 downto 4),b(7 downto 4),s(7 downto 4),m1,m2);
u3:adder_4 port map(a(11 downto 8),b(11 downto 8),s(11 downto 8),m2,m3);
u4:adder_4 port map(a(15 downto 12),b(15 downto 12),s(15 downto 12),m3,cout);
end architecture behave;

```

```

-----adder_tb.vhd-----

library ieee;
use ieee.std_logic_1164.all;
-----

entity adder_tb is
end adder_tb;
-----

architecture adder_tb of adder_tb is
component adder
    port (a,b:in std_logic_vector(15 downto 0);
        cin:in std_logic;
        s:out std_logic_vector(15 downto 0);
        cout: out std_logic);
end component;
-----

signal a,b: std_logic_vector(15 downto 0);

```

```

signal cin:std_logic;
signal s:std_logic_vector(15 downto 0);
signal cout:std_logic;

begin
dut:adder port map
(a(15 downto 0)=>a(15 downto 0),b(15 downto 0)=>b(15 downto 0),cin=>cin,s(15 downto
0)=>s(15 downto 0),cout=>cout);
-----


a_gen:process
begin
    a<="0000000000000000";
    wait for 400 ns;
    a<="1111111111111111";
    wait for 400 ns;
    a<="0101010101010101";
    wait for 400 ns;
    a<="1111000011110000";
    wait for 400 ns;
end process;
-----

b_gen:process
begin
    b<="0000000000000000";
    wait for 400 ns;
    b<="1111111111111111";
    wait for 400 ns;
    b<="1010101010101010";
    wait for 400 ns;
    b<="0000111100001111";
    wait for 400 ns;
end process;
-----

cin_gen:process
begin
    cin<='0';
    wait for 200 ns;
    cin<='1';
    wait for 200 ns;
end process;
end adder_tb;
-----

```

四、仿真结果

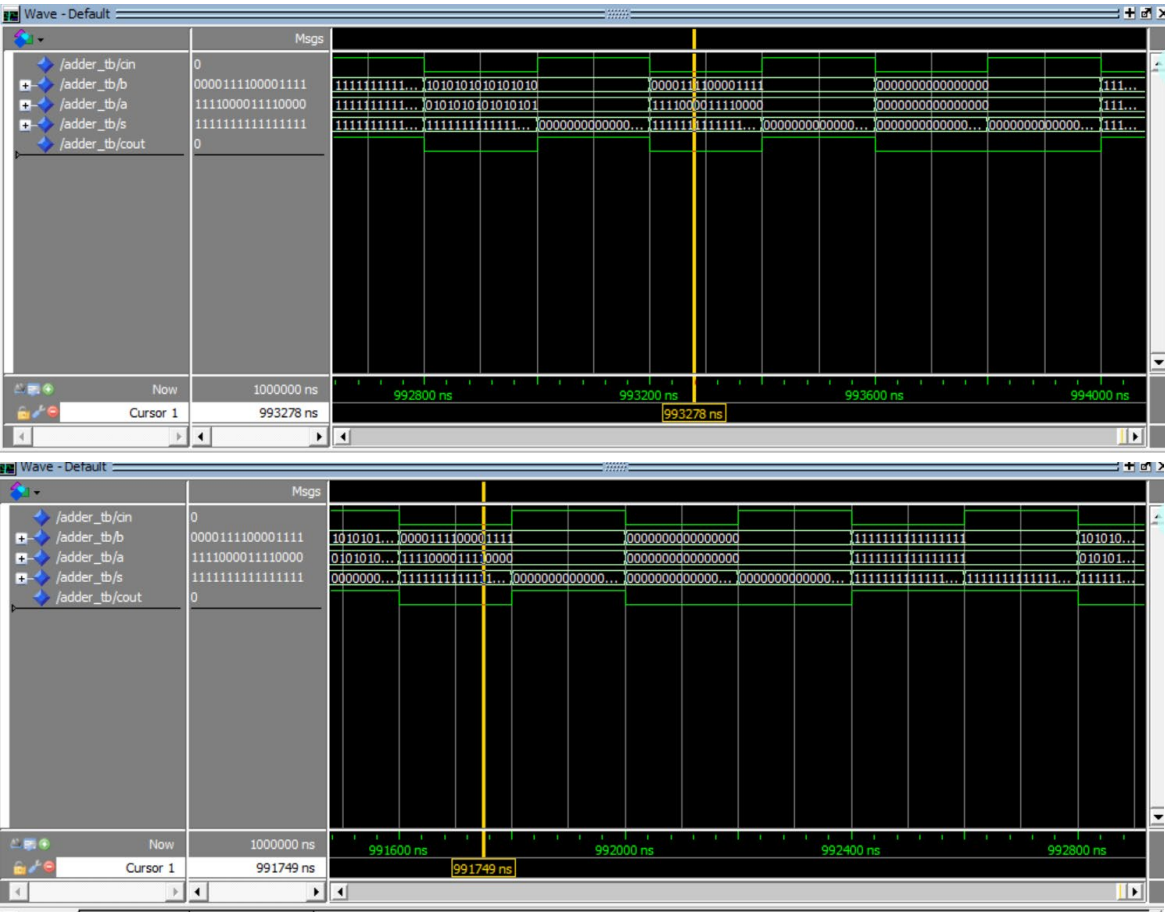

五、分析与总结

从结果我们可以看出，当 cin 为 1 的时候，若不发生最高位进位（即 cout≠1），则此时的运算结果（可以转化为十进制数据类型）是正确的，当不发生最高位进位时，结果与预期一致。

总的来说，利用 4 位超前进位加法实现了 16 位超前进位加法的功能。